

Figure 1 - differential amplifier

### Design

The current mirrors realised with Q3 and Q4 transistors bias the differential amplifiers transistors T1 and T2 at:

$$-I_{C1,2} \cdot R_4 - V_{BE} + V_{DZ} = 0$$

$$I_{C1} = I_{C2} = \frac{(V_{DZ} - V_{BE})}{R_4} = \frac{(1.22 - 0.6)}{2e3} \approx 0.3 \text{ mA}$$

We can see that for a differential drive at the input, the applied voltages on the bases of T1 and T2 and found at their emitters are equal in magnitude but opposite in phase. We can consider that the potential at the median point of R3 resistor stays unchanged. So, the median point of R3 is a virtual common point, which drives to the drawing of the equivalent differential schematic of the amplifier illustrated in Figure 2:

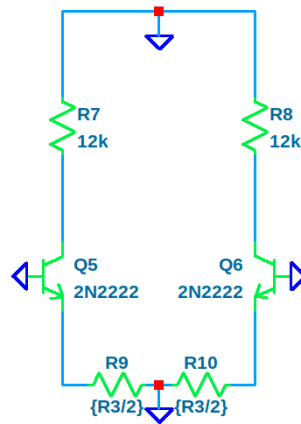


Figure 2

The differential gain is calculated using the half-circuit available for the differential amplifier, Figure 3:

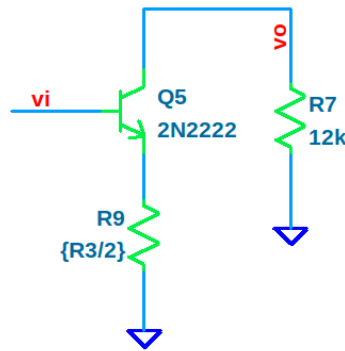


Figure 3

$$A_v = A_{dd} = V_{od}/V_{id} = -\beta R_l / [r_\pi + (\beta + 1) \cdot R_3/2]$$

where  $R_l = R_C \parallel R_{01}$ ,  $R_{01}$  being the output resistance of the stage.  $R_{01}$  is enlarged as against to  $r_{01}$  because of the external emitter resistance.

$$R_{01} \approx r_{01} (1 + gm \cdot (R_3/2 + r_\pi))$$

Knowing that in the quiescent point  $I_{C1} \sim 0.3 \text{ mA}$  we can find the equivalent transistor parameters:

$$gm = I_C / (kT/q) = 300e-6 / 26e-3 = 11.3e-3 \text{ A/V}$$

$$r_\pi = \beta / gm = 200 / 11.3e-3 = 17.7 \text{ e } 3 \Omega$$

$$r_{01} = r_0 \big|_{at 1 \text{ mA}} 1 \text{ mA} / 0.3 \text{ mA} = 101e3 \cdot (1/0.3) = 336 \text{ e } 3 \Omega$$

$$\text{where } r_0 = \frac{1}{(\eta \cdot gm)}$$

now we can get

$$R_{01} = 336e3(1 + 11.3e-3(1e3 + 17.7e3)) = 71e6\Omega$$

$$R_l = R_{01} \parallel R_C \approx R_C = 12k\Omega$$

which drives to

$$A_v = A_{dd} = V_{od}/V_{id} = -R_l/(R_3/2) = -12$$

For the common mode gain we start from the observation that having a common mode excitation, through R3 resistance in Figure 1, does not flow any current, so this resistance can be considered an open circuit. This observation permits to draw the half-circuit available for the common mode in Figure 4 in R<sub>03</sub> is the resistance seen in the collector of T3. Solving for this resistance in the same way as for the R<sub>01</sub> resistance we have:



Figure 4

$$R_{03} \approx r_{03}(1 + gm \cdot (R_4 + r_{\pi})) = 336e3(1 + 11.3e-3(2e3 + 17.7e3)) = 71e6\Omega$$

$$A_{cc} = V_{oc}/V_{ic} = -R_C/R_{03} = 571e-6$$

### Simulation

Add (for a 1 mV differential signal):



Also taking into account the differential excitation of the stage, we find in the T2 collector a current equal in magnitude with  $I_C$ , but of opposite phase as we see in Figure 7:

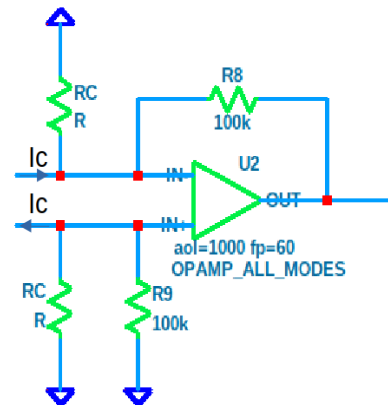


Figure 7

We will take U1 as an ideal operational amplifier, its positive and negative input potentials relative to ground must be equal:

$$V_+ = V_-$$

$V_+$ , the noninverting input voltage relative to ground is:

$$-V_+ - I_C(R_C \parallel R_9) = 0$$

$V_-$ , can be found out by applying superposition theorem, finding immediately

$$V_- = I_C(R_C \parallel R_8) + V_O(R_C / (R_C + R_8))$$

From  $V_+ = V_-$  we get:

$$-I_C(R_C \parallel R_9) = I_C(R_C \parallel R_8) + V_O(R_C / (R_C + R_8)) \text{ where } R_8 = R_9$$

or

$$2I_C = -(V_O / R_8)$$

and knowing that  $I_C = V_i / R_3$  we get

$$\frac{V_O}{V_i} = -2 \frac{R_8}{R_3}$$

For  $R_8 = 100k$  and  $R_3 = 2k$  we have  $A_{dd} = -100$ .

### Simulation

For  $V_i = 1 \text{ mV}$ :

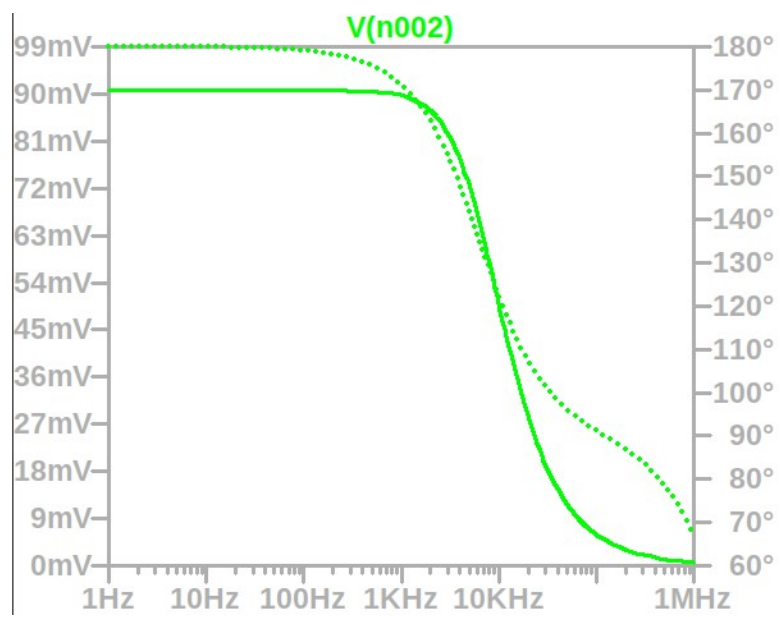


Figure 8