

Design Example: CMOS Differential-pair with Constant-gm Biasing

Biased, FREEPDK45

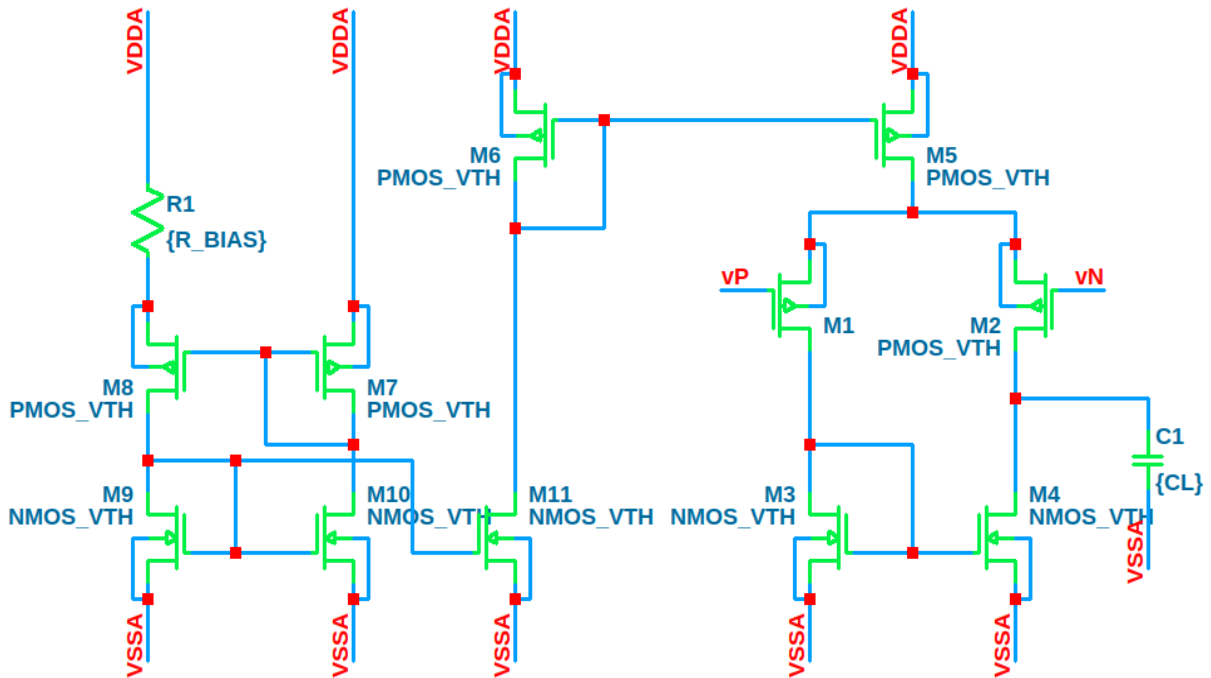


Figure 1: Diff-pair with Constant-gm Biasing

Specifications:

VDD = 1.8V, GBW = 120e6 Hz, $C_L = 10$ pF, with freePDK45 process node technology

$$-V_P - V_{SG} - V_{SDsat} + V_{DDA} = 0 \text{ and } -V_P - V_{SG} + V_{SDsat} + V_{GS} = 0$$

$$V_{GS} - V_{SG} + V_{SDsat} < V_{IN,CM} < V_{DDA} - V_{SG} - V_{SDsat}$$

→ Start with M1 (and M2)

- From C_L and GBW: $g_{m,M1} = 2\pi f_u (1+0.2) C_L = 2\pi \cdot 120e6 \cdot 1.2 \cdot 10e-12 = 9.04e-3$ S, where the factor 0.2 is to capture some parasitic capacitance

- Since we don't have a specific power consumption spec here, we pick $g_m/I_D = 15$ (mS/μA) for M1 since it is a gain stage

$$I_D = \frac{g_{m,M1}}{g_m/I_D} = \frac{9e-3}{15} = 603.18 \mu A$$

- From I_D/W vs g_m/I_D plot (LUT) of PMOS, we determine (there could be some other different candidates)

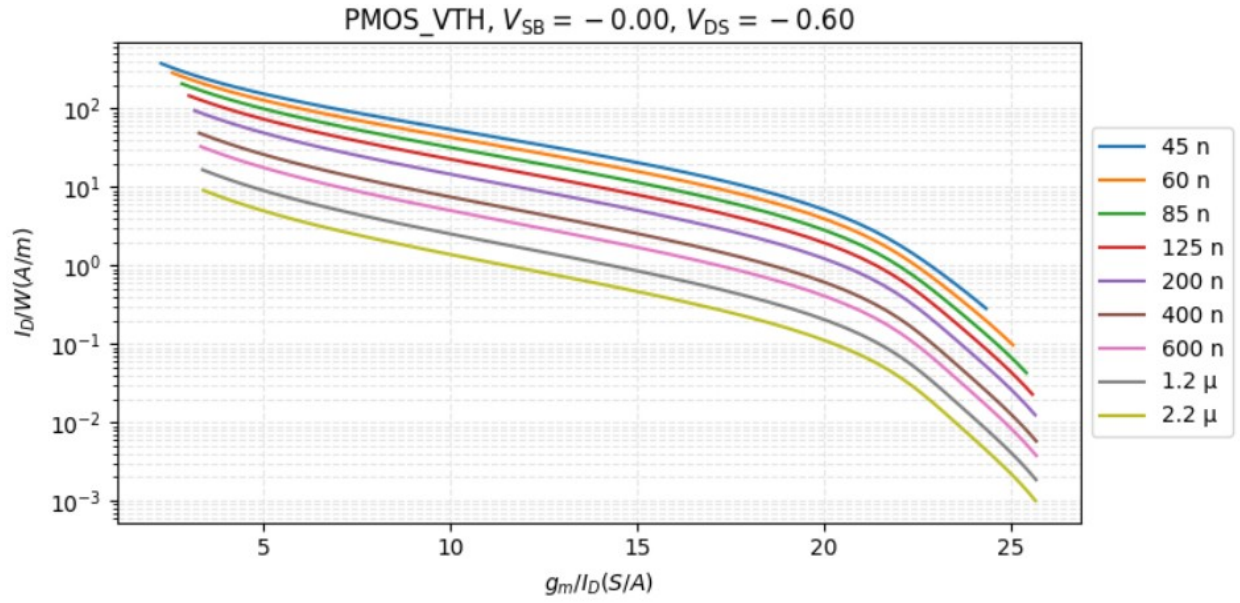


Figure 2: I_D/W vs g_m/I_D plot (LUT) of PMOS

for $L=125\text{ nm}$, $g_m/I_D=15$ we have $\frac{I_D}{W}=7.96$

$$W_{M1} = \frac{I_D}{J_D} = \frac{603\text{e-}6}{7.96} = 75.75\text{ }\mu\text{m}$$

(If you have any DC gain requirement, you can increase L_{M1} by looking at g_m/g_{ds} vs. g_m/I_D plot, which will give you a new W_{M1} .)

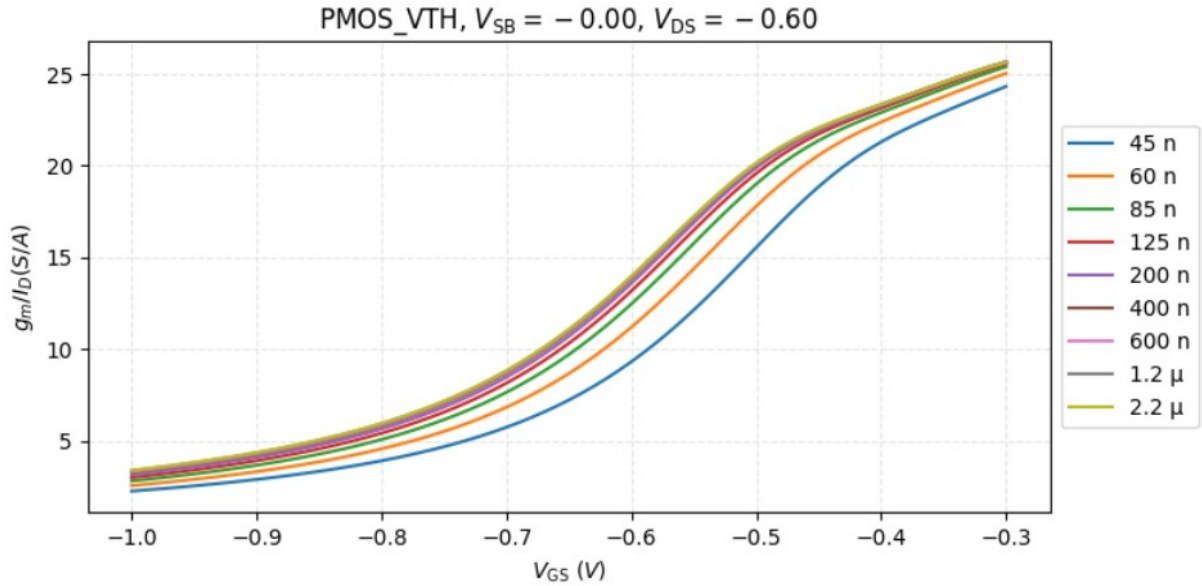


Figure 3: g_m/I_D vs V_{SG}

from $g_m/I_D=15$ vs V_{GS} for $L=125\text{ nm} \rightarrow V_{GS}=-0.572\text{ V}$

→ Second, we design M3 (and M4)

- Since we don't have a specific power consumption spec here, we pick $g_m/I_D = 10$ for M3 since it is an active load (source), so it should be smaller
- Since we know $I_{D,M3} = I_{D,M1} = 603 \mu A$ already from the calculation of M1, from I_D/W vs g_m/I_D plot (LUT) of NMOS, we determine (there could be some other candidates)

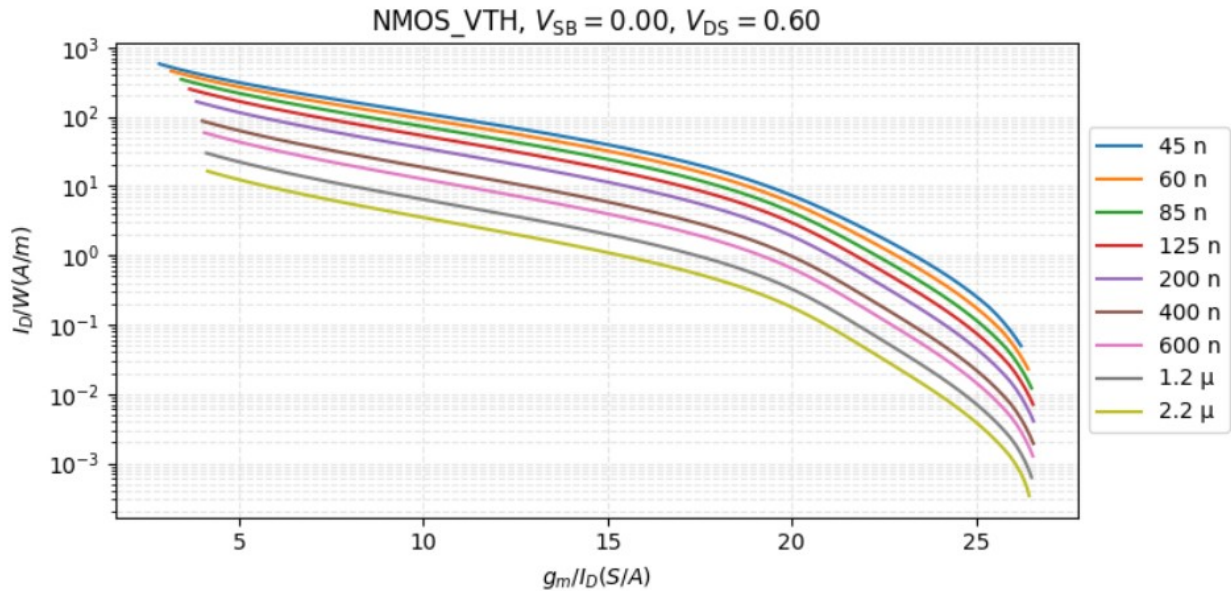


Figure 4: I_D/W vs g_m/I_D plot (LUT) of NMOS

for $L = 600 \text{ nm}$, $g_m/I_D = 10$, we have $I_D/W = 12.54$

$$W_{M3} = \frac{I_D}{J_D} = \frac{603 \text{e-}6}{12.54} = 48.08 \mu\text{m}$$

The active load and current source should have larger output impedance, therefore L is intentionally picked larger value.

→ Third, we design current mirror M5 (and M6)

- For simplicity here, we assume M5 and M6 have the same dimension (can be scaled down later for reducing power consumption)
- Since we don't have a specific power consumption here, we pick $g_m/I_D = 4$ for M5 since it is active load (source), a device whose g_m does not contribute to gain and should have a good matching we pick the transconductance efficiency in SI (The mismatch is independent of transistor width in strong inversion. The only way to improve the matching is to employ a longer channel.)

The g_m/I_D is even smaller than M3's since here, $I_{D,M5} = 2 I_{D,M3}$, smaller g_m/I_D can give larger L values, which is desirable for current mirror design

- Since we know $I_{D,M5} = 2 I_{D,M1} = 1.2 \text{e-}3 \text{ A}$, already from the calculation of M1, from I_D/W vs g_m/I_D plot (LUT) of PMOS Figure 2 we determine (there could be some other different candidates)

for $L=1.2\text{e-}6$, $g_m/I_D=4$ we have $I_D/W=12.93$

$$W_{M5,6} = \frac{I_D}{J_D} = \frac{1.2\text{e-}3}{12.93} = 92.8 \text{ } \mu\text{m}$$

Now, we can start designing the constant-gm biasing block

Analysis:

→ NMOS implementation of constant- g_m biasing circuit

 


Figure 5: NMOS implementation

→ PMOS implementation of constant- g_m biasing

 


Figure 6: PMOS implementation

Analysis:

 


Figure 7: G_m of NMOS with R_B in source

→ an analysis of the M15 and R_B subcircuit from Figure 5, shown in Figure 7 will show that G_m of this circuit is equal to $1/R_B$

$$G_m = \frac{i_{out}}{v_{in}}$$

$$i_{out} - gm v_{gs} = 0 \rightarrow i_{out} = gm v_{gs}$$

$$-R_B i_{out} - v_{gs} + v_{in} = 0 \rightarrow v_{in} = R_B i_{out} + v_{gs}$$

$$\rightarrow G_m = \frac{gm v_{gs}}{R_B i_{out} + v_{gs}} = \frac{gm v_{gs}}{R_B gm v_{gs} + v_{gs}} \approx 1/R_B$$

→ to keep gm constant in Figure 5 we need $gm_{13} = 1/R_B$, this way if we can select gm through g_m/I_D , we can set R_B to give us a specific current for biasing our amplifier

Now we will analyse Figure 5, to get the needed aspect ratios to have $gm_{13} = 1/R_B$:

$$-R_B I_{D15} - V_{GS15} + V_{GS13} = 0$$

$$V_{GS} = V_T + \sqrt{\frac{2I_D}{k'_n \frac{W}{L}}}, \text{ strong inversion, square-law design}$$

$$\text{if } I_{D15} = I_{D13}$$

$$R_B I_D = \sqrt{\frac{2 I_D}{k'_n \frac{W_{13}}{L_{13}}}} - \sqrt{\frac{2 I_D}{k'_n \frac{W_{15}}{L_{15}}}}$$

we need $g_m = \sqrt{2 \mu C_{ox} \frac{W}{L} I_D} = \frac{1}{R_B}$ in strong inversion, with square-law design

$$R_B I_D = \sqrt{2 I_D} \left(\frac{1}{\sqrt{k'_n \frac{W_{13}}{L_{13}}}} - \frac{1}{\sqrt{k'_n \frac{W_{15}}{L_{15}}}} \right)^2$$

$$\rightarrow R_B^2 I_D^2 = 2 I_D \left(\frac{1}{k'_n \frac{W_{13}}{L_{13}}} + \frac{1}{k'_n \frac{W_{15}}{L_{15}}} - 2 \frac{1}{k'_n \sqrt{\frac{W_{13}}{L_{13}} \frac{W_{15}}{L_{15}}}}} \right) \cdot k'_n$$

$$\rightarrow k'_n R_B^2 I_D = 2 \left(\frac{1}{\frac{W_{13}}{L_{13}}} + \frac{1}{\frac{W_{15}}{L_{15}}} - 2 \frac{1}{\sqrt{\frac{W_{13}}{L_{13}} \frac{W_{15}}{L_{15}}}}} \right)$$

here the right hand element, i.e., $2 \left(\frac{1}{\frac{W_{13}}{L_{13}}} + \frac{1}{\frac{W_{15}}{L_{15}}} - 2 \frac{1}{\sqrt{\frac{W_{13}}{L_{13}} \frac{W_{15}}{L_{15}}}}} \right)$, must be equal to $\frac{1}{2 \frac{W_{13}}{L_{13}}}$

$$\text{so that } g_m = \sqrt{2 \mu C_{ox} \frac{W}{L} I_D} = \frac{1}{R_B}$$

$$\rightarrow 2 \left(\frac{1}{\frac{W_{13}}{L_{13}}} + \frac{1}{\frac{W_{15}}{L_{15}}} - 2 \frac{1}{\sqrt{\frac{W_{13}}{L_{13}} \frac{W_{15}}{L_{15}}}}} \right) = \frac{1}{2 \frac{W_{13}}{L_{13}}}$$

and after further algebraic analysis we find $4 \frac{W_{13}}{L_{13}} = \frac{W_{15}}{L_{15}}$

$$\rightarrow k'_n R_B^2 I_D = 2 \left(\frac{1}{\frac{W_{13}}{L_{13}}} + \frac{1}{4 \frac{W_{13}}{L_{13}}} - 2 \frac{1}{\sqrt{\frac{W_{13}}{L_{13}} 4 \frac{W_{13}}{L_{13}}}}} \right)$$

$$\rightarrow k'_n R_B^2 I_D = 2 \left(\frac{4+1}{4 \frac{W_{13}}{L_{13}}} - 2 \frac{1}{2 \frac{W_{13}}{L_{13}}} \right) = \frac{10}{4 \frac{W_{13}}{L_{13}}} - \frac{2}{\frac{W_{13}}{L_{13}}} = \frac{10-8}{4 \frac{W_{13}}{L_{13}}} = \frac{1}{2 \frac{W_{13}}{L_{13}}}$$

$$\rightarrow 2 k'_n \frac{W_{13}}{L_{13}} I_D = \frac{1}{R_B^2} \rightarrow \sqrt{2 k'_n \frac{W_{13}}{L_{13}} I_D} = \frac{1}{R_B}$$

We arrive at, $g_{m,M7} = 1/R_{BIAS}$ if $W_{M8} = 4 W_{M7}$, where this were calculated as with long channels and strong-inversion equations.

If we let M1 and M7 have the same size, and if we can somehow let M1 and M7 have the same g_m , then their I_D will also be the same.

Design R_{BIAS} :

$$\text{Letting } g_{m1} = g_{m7} : g_{m1} = g_m / I_D \cdot I_{d,M1} = 9e-3 S$$

$$R_{BIAS} = \frac{1}{g_{m7}} = 111 \Omega$$

→ Design M7 (and M8)

- Simply copying M1 to M7: $W_{M1} = W_{M7} = 75.75 \mu m ; L_{M1} = L_{M7} = 125 nm$

- Rather than making $W_{M8} = 4 W_{M7}$, we can let $W_{M8} = W_{M7}$ and use multiplier $M_{M8} = 4 M_{M7}$ (you can approximate its value by SPICE simulations, as the equations used for this example are not accurate)

→ Design M9 (M10 and M11)

- Simply copying M3 to M9, M10

- For M11 we simply double the width of M9

- If necessary you can increase L of M9, M10 and M11 to increase the output resistance of current mirror, ensuring you are always operating them in saturation region.

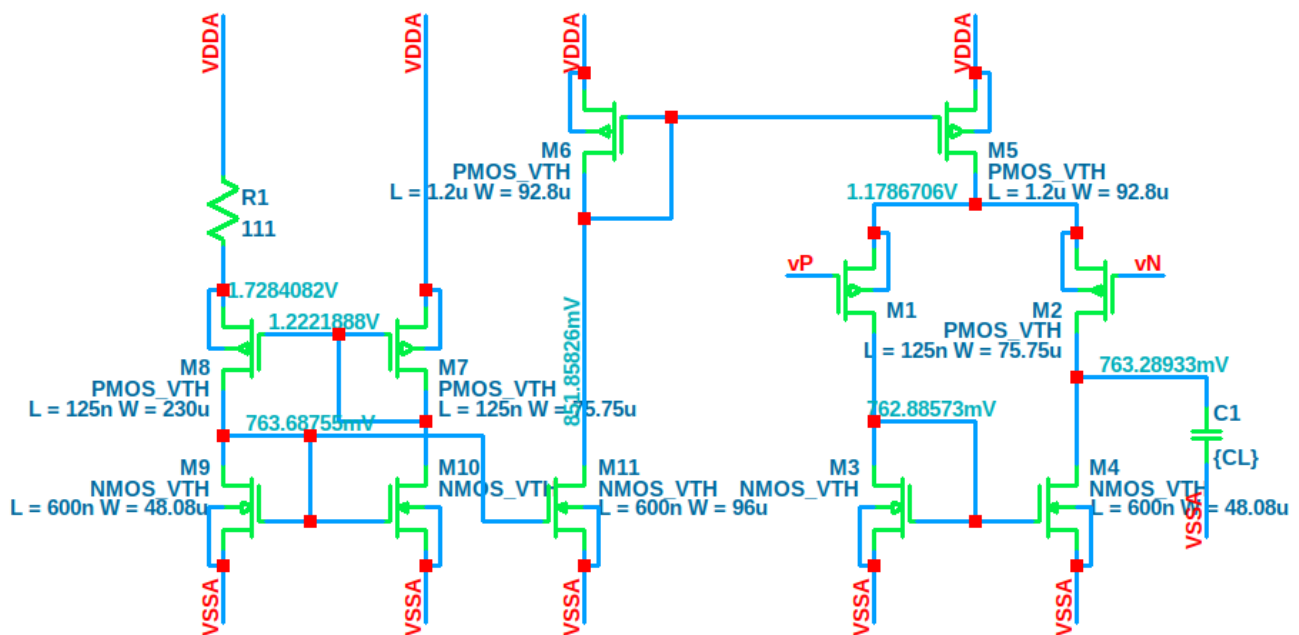


Figure 8: Diff-Amp with Aspect Ratios for GBW ~120 MHz with freePDK45

 


Figure 9: GBW representation ~ 120 MHz

Appendix

Note: If you are designing by A_{v0} as a specification parameter, then L and g_m/I_D will play a significant role as seen in Figure 10, where

$$A_{v0} = \frac{g_{m1}}{g_{ds2} + g_{ds4}}$$

$$\rightarrow A_{v0} = \frac{\frac{g_{m1}}{I_D} I_D}{\frac{g_{ds2}}{I_D} + \frac{g_{ds4}}{I_D}}$$

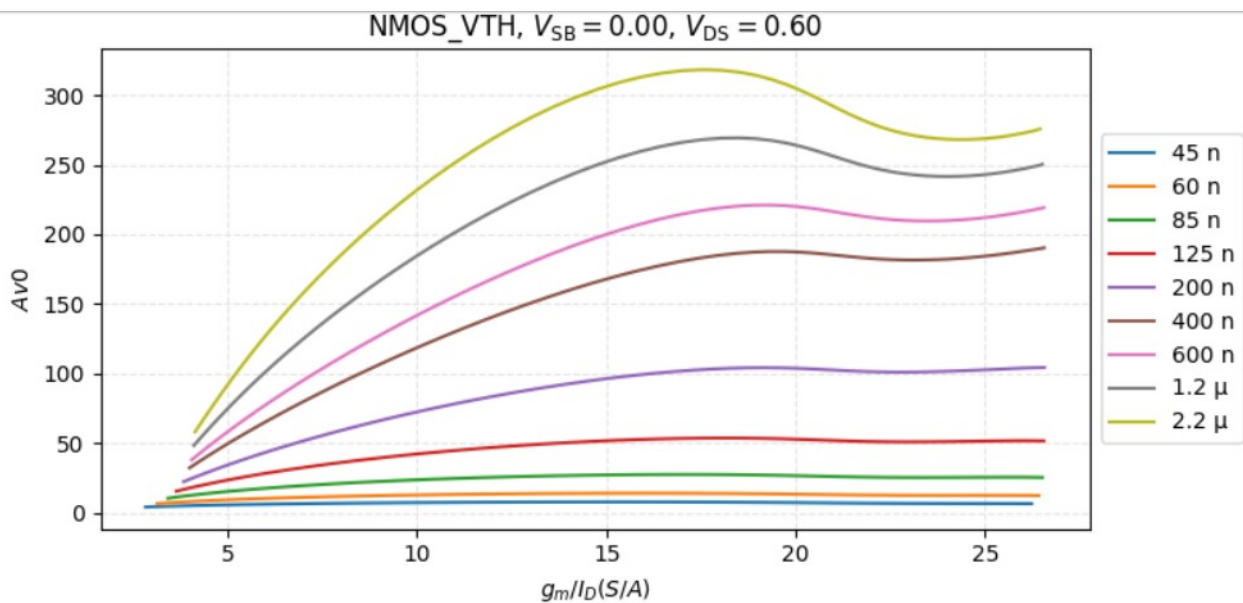


Figure 10: A_{v0} vs (g_m/I_D)

A_{v0} will also tradeoff with f_t Figure 11, and implicitly f_u of the circuit:

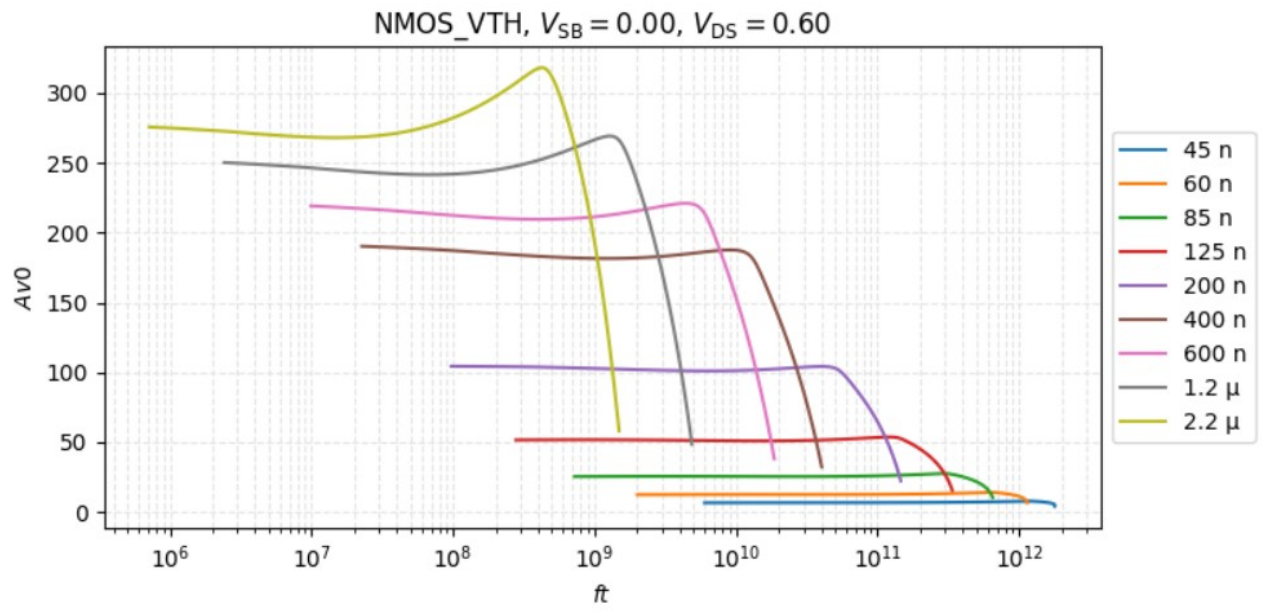


Figure 11: A_{v0} vs f_t