

Analysis

$V_A - V_B$ potential difference is given by:

$$-V_A - V_{GS3} + V_{GS4} + V_B = 0$$

$$\text{then } V_A - V_B = V_{GS4} - V_{GS3} = \left(V_T + \sqrt{\frac{2I_{D4}}{K_4}} \right) - \left(V_T + \sqrt{\frac{2I_{D3}}{K_3}} \right) = \sqrt{\frac{2I_{D4}}{K_4}} \left(1 - \sqrt{\frac{I_{D3}}{I_{D4}} \frac{K_4}{K_3}} \right)$$

$$\text{where } K = \mu C_{ox} \frac{W}{L}$$

Because of the current mirror M5 – M6 we can write:

$$\frac{I_{D3}}{I_{D4}} = \frac{I_{D5}}{I_{D6}} = \frac{K_5}{K_6}$$

$$\text{so } V_A - V_B = \sqrt{\frac{2I_{D4}}{K_4}} \left(1 - \sqrt{\frac{K_5}{K_6} \frac{K_4}{K_3}} \right)$$

The condition to make the $V_A - V_B$ difference equal to zero is:

$$K_4 K_5 = K_3 K_6$$

equivalent with:

$$\left(\frac{W}{L} \right)_4 \left(\frac{W}{L} \right)_5 = \left(\frac{W}{L} \right)_3 \left(\frac{W}{L} \right)_6$$

Because $K_4 K_5 = K_3 K_6$, $V_A = V_B$ we get:

$$-V_{EB1} + I_3 R_3 = 0 \rightarrow I_3 = I_4 = \frac{V_{EB1}}{R_{3,4}}$$

I_1 current expression is given by:

$$-V_{EB2} - I_1 R_1 + V_{EB1} = 0 \rightarrow I_1 = \frac{V_{EB1} - V_{EB2}}{R_1} = \frac{kT}{q R_1} \ln \left(\frac{I_{S2}}{I_{S1}} \frac{I_{C1}}{I_{C2}} \right)$$

Knowing:

$$I_{D5} - I_3 - I_{C1} = 0 \rightarrow I_{C1} = I_{D5} - I_3$$

and:

$$I_{D6} - I_4 - I_{C2} = 0 \rightarrow I_{C2} = I_{D6} - I_4$$

with T_5 and T_6 being identical, $I_{D5} = I_{D6}$ so $I_{C1} = I_{C2}$, resulting:

$$I_1 = \frac{kT}{q R_1} \ln \left(\frac{I_{S2}}{I_{S1}} \right)$$

The reference voltage V_{ref} is:

$$V_{Ref}(T) = (I_1 + I_4) R_2 = \frac{R_2}{R_1} \frac{kT}{q} \ln \left(\frac{I_{S2}}{I_{S1}} \right) + \frac{R_2}{R_4} V_{EB1}(T)$$

$$V_{Ref}(T) = \frac{R_2}{R_1} \frac{kT}{q} \ln \left(\frac{I_{S2}}{I_{S1}} \right) + \frac{R_2}{R_4} \left[E_{G0} + \frac{V_{BE}(T_0) - E_{G0}}{T_0} T + (1 - \eta) \frac{kT}{q} \ln \left(\frac{T}{T_0} \right) \right]$$

To produce a correction of first order on the temperature characteristic voltage reference, implies to cancel the linear temperature dependent parameters:

$$\frac{k}{q R_1} \ln \left(\frac{I_{S2}}{I_{S1}} \right) + \frac{V_{BE}(T_0) - E_{G0}}{R_4 T_0} = 0$$

Giving us:

$$V_{Ref}(T) = \frac{R_2}{R_4} \left[E_{G0} + (1 - \eta) \frac{kT}{q} \ln \left(\frac{T}{T_0} \right) \right]$$

Design

All MOS transistors have identical aspect ratios, the bipolar saturation currents ratio $I_{S2}/I_{S1} = 100$, $V_{EB1}(T_0) = 0.6$ V, $R_3 = R_4$.

The linear temperature correction characteristic of V_{ref} implies respecting the following relation:

$$\frac{k}{q R_1} \ln \left(\frac{I_{S2}}{I_{S1}} \right) + \frac{V_{BE}(T_0) - E_{G0}}{R_4 T_0} = 0$$

$$\text{from which we get } \frac{R_4}{R_1} = \frac{E_{G0} - V_{BE}(T_0)}{\frac{k T_0}{q} \ln \left(\frac{I_{S2}}{I_{S1}} \right)} = \frac{1.2 - 0.6}{\frac{1.38e-23 \cdot 273}{1.6e-19} \ln(100)} = 5.54$$

Selecting $R_1 = 8k$ we get

$$R_4 = 5.54 \cdot 8e3 = 44e3 \Omega$$

From the voltage – current relationship of MOS transistors in saturation we get:


$$I_{D3,4} = \frac{K_n'}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$I_{D5,6} = \frac{K_p'}{2} \frac{W}{L} (V_{SG} - |V_T|)^2$$

$$\frac{W}{L} = \frac{2I_D}{K'(V_{GS} - V_T)^2}$$

→ an easier way to design is by using NMOS and PMOS references

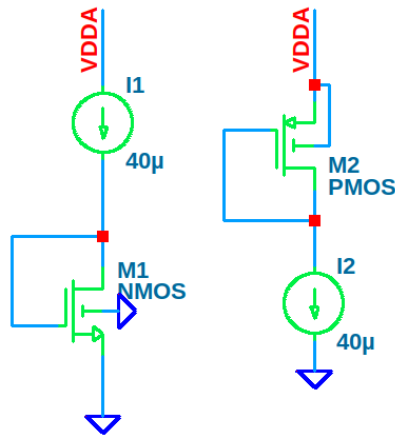We will start by using the following reference set (MOSFET model file 180 nm TSMC process):



The references have been selected to have the following characteristics:

	NREF	PREF
L [m]	180e-9	180e-9
W [m]	2e-6	6e-6
ID [A]	40e-6	40e-6
Vov [V]	127e-3	153e-3
Vth [V]	486e-3	520e-3
Gm [A/V]	496e-6	447e-6
Rds [Ohm]	80.6e3	108e3

We want to design for:

	NMOS	PMOS
L [m]	2e-6	2e-6
ID	32e-6	32e-6
Vov	140e-3	140e-3

Using our references we get the following parameters:

	NMOS	PMOS
L [m]	2e-6	2e-6
W [m]	14.6e-6	63.7e-6
ID [A]	32e-6	32e-6
Vov [V]	140e-3	140e-3
Gm [A/V]	360e-6	390e-6

SPICE simulation gives us:

	NMOS	PMOS
L [m]	2e-6	2e-6
W [m]	14.6e-6	63.7e-6
ID [A]	34e-6	34.7e-6
Vov [V]	161e-3	156e-3
Gm [A/V]	365e-6	358e-6


Note that here we will use for all transistors the same aspect ratio. (PMOS or NMOS transistor width can be further refined to have identical dc currents)

From I_1 equation we can see that the temperature dependence of it is linear:

$$I_1(T) = AT$$

'A' being a constant of value:
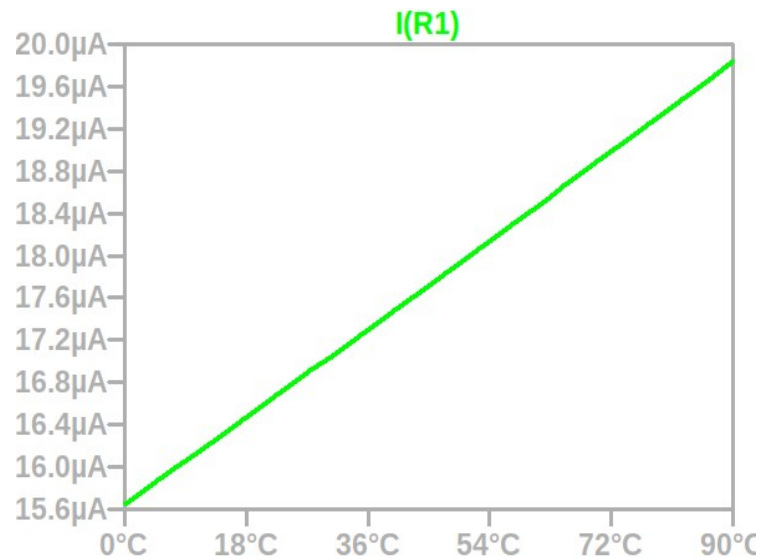
$$\text{from } I_1 = \frac{kT}{qR_1} \ln\left(\frac{I_{S2}}{I_{S1}}\right) \text{ we have } A = \frac{k}{qR_1} \ln\left(\frac{I_{S2}}{I_{S1}}\right) = \frac{1.38e-23}{1.6e-19 \cdot 8e3} \ln(100) = 49.6 \text{ nA/K}$$



From the simulation we get $A = 47.97 \text{ nA/K}$. (I_1 is PTAT, whereas I_4 is CTAT and both cancel each other)

Selecting the R_4/R_1 ratio derived earlier, from simulation we can also see that the temperature dependence of the voltage reference will depend only on the logarithmic equation:

