

LDO_A (FREEPDK45) Design using LUT

 


Figure 1: LDO with series-transistor

 


Figure 2: LDO SS

low-frequency analysis

This LDO have a series-shunt feedback loop (with the first term referring to the input), with a feedback transfer function f of 1, and the closed-loop transfer function is:

$$\frac{V_{out}}{V_{ref}} = \frac{A_1 A_a}{1 + A_1 A_{ref} f}$$
, where A_1 and A_a are the voltage gains of the CS series transistor and the differential amplifier, respective.

$$\text{loop-gain} = 1 + A_1 A_{ref} f$$

Specifications

$$I_{DC} = 10 \text{ mA}, V_{OUT} = .9 \text{ V}, VDD = 1.2 \text{ V size for the highest loop-gain}$$

Matlab

```
VDD = 1.2;           % supply voltage
V = .9;              % desired regulated voltage
ID = .01;            % desired current (RL = V/ID)
L = 100e-9;
Lp = 400e-9;
Ln = 400e-9;
```

Solution

CS

$$A_{1DC} = \frac{g_{m1}}{Y_L + g_{ds1}} = \frac{\left(\frac{gm}{id}\right)_1}{\frac{1}{V_{OUT}} + \left(\frac{gds}{id}\right)_1}$$

$$V_{Dsat} = \frac{2}{\frac{g_m}{id}}, \text{ we need to keep } gm/id \text{ larger than } 6.6 \text{ S/A to keep } V_{dsat} \text{ of M1}$$

smaller than the dropout voltage (0.3 V).

Matlab

```
for i = 7:12
    gm_id = i;

    VDS = V-VDD;
    gds_id = lookup_data(my_mat.pmos, 'gds_id', 'gm_id', gm_id, 'vds', VDS, 'lengths', L);
    JD = lookup_data(my_mat.pmos, 'id_width', 'gm_id', gm_id, 'vds', VDS, 'lengths', L);
    A = gm_id./(1/V + gds_id);

    W = ID/JD;
    Cgs = abs(W*lookup_data(my_mat.pmos, 'cgs_width', 'gm_id', gm_id, 'vds', VDS, 'lengths', L));
    Cgd = abs(W*lookup_data(my_mat.pmos, 'cgd_width', 'gm_id', gm_id, 'vds', VDS, 'lengths', L));
    VGS = lookupVGS(my_mat.pmos, 'gm_id', gm_id, 'vds', VDS, 'lengths', L);

    gm = gm_id*ID;
    gds = gds_id*ID;
    YL = ID/V;

    %disp("gm_id");
    %disp(gm_id); % and so on
end
```

To select $(gm/id)_1$ we will have to enumerate the gains of the stage for different values of $(gm/id)_1$ between 7 S/A and 12 S/A. In the following table the top entries are for $L_1 = 100\text{nm}$, the bottom entries for $L_1 = 200\text{ nm}$.

$(gm/id)_1 S/A$	7	8	9	10	11	12
A_1	4.5	5.34	6.09	6.8	7.4	8.1
	4.97	5.95	6.88	7.78	8.65	9.5
$W_1(\mu m)$	198	244	299	365	445	542
	373	465	575	709	870	1069
V_{GS1}	-.72	-.69	-.67	-.65	-.63	-.61
	-.74	-.71	-.68	-.664	-.644	-.626
C_{gs1}	3.7e-13	4.5e-13	5.3e-13	6.2e-13	7.2e-13	8.3e-13
	1.4e-13	1.7e-13	2e-12	2.4e-12	2.8e-12	3.3e-12
C_{gd1}	3.6e-15	4.55e-15	5.6e-15	6.7e-15	8e-15	9.4e-15
	2.8e-15	1.76e-15	e-16	3.6e-15	1.4e-15	2.6e-15

Going to 200nm improves the gain very little and is very costly as far as layout area is concerned. We conclude that a gm/id of 10 with L1 = 100nm gives a good compromise.

Differential-Pair Amplifier Sizing

$$A_a = \frac{\left(\frac{g_m}{id}\right)_n}{\left(\frac{g_{ds}}{id}\right)_n + \left(\frac{g_{ds}}{id}\right)_p}$$

The drain to source and the gate-to source voltages of the p-channel mirror devices are fixed by VGS1 and hence the gate length is the only degree of freedom for their sizing. Since we value gain more than bandwidth in this sub-circuit, we opt for 400nm channel length, and this allow us to find (gds/id)p.

```
gds_idp = lookup_data(my_mat.pmos, 'gds_id', 'vgs', VGS, 'vds', VGS, 'lengths', Lp);
```

For the diff-pair, for high gain we assume L = 400nm, and to find the maximum Aa we will use the following Matlab script in which we iterate over available VS the gain of the differential pair:

Matlab

```
VD = VDD - abs(VGS);
US = (.2: .015: .5)'; zn = length(US);
for k=1:zn
    VS = US(k);
    gm_idn(k,1) = lookup_data(my_mat.nmos, 'gm_id', 'vgs', V-VS, 'vds', VD-VS, 'vsb', VS, 'lengths', Ln);
    gds_idn(k,1) = lookup_data(my_mat.nmos, 'gds_id', 'vgs', V-VS, 'vds', VD-VS, 'vsb', VS, 'lengths', Ln);
end

Aa = gm_idn./(gds_idn + gds_idp);
```

And now we can plot the loop-gain:

```
f = 1;  
loop_gain = Aa.*A*f;  
  
plot(gm_idn, loop_gain)  
xlabel('gm/idn');  
ylabel('loop-gain');
```

 


Figure 3: Loop-gain vs $(gm/id)_n$

From Figure 3 we see that the maximum loop-gain that we get with this circuit can be achieved by using $(gm/id)_n$ equal to 20.

By interpolation we can find Aa and Vs (the source voltage):

```
value_of_Aa_for_gm_idn_20 = interp1(gm_idn, Aa, 20)
```

```
VS = interp1(gm_idn, US, 20)
```

```
gds_IDN = interp1(gm_idn, gds_idn, 20)
```

Where we get Aa = 164.82, VS = 0.27V. Based on the data, we make the following design choices:

- series transistor L1 = 100nm, $(gm/id)_1 = 10$ S/A
- differential amplifier Ln = 400nm with $(gm/id) = 20$ S/A
- the loop-gain is 1121 with A1 = 6.8 and Aa = 164.82

Now we need to decide for the tail current.

The amplifier bias current is normally a small fraction of the LDO's output current. We push 2% in this example, which leads to $2I_{Dn} = 0.2 \text{ mA}$. This choice lets us finalize the sizing for the SPICE verification.

Matlab

```
IDN = 100e-6;
JDP = lookup_data(my_mat.pmos, 'id_width', 'vgs', VGS, 'vds', VGS, 'lengths', Lp);
Wp = IDN/JDP;
JDN = lookup_data(my_mat.nmos, 'id_width', 'vgs', V-VS, 'vds', VD-VS, 'vsb', VS, 'lengths', Ln);
Wn = IDN/JDN;

gda = (gds_idp + gds_IDN)*IDN;           %output conductance of diff amplifier
gma = gm_IDN*IDN;
```

The resulting widths are:

$W_n = 102 \text{ um}$

$W_p = 15.8 \text{ um}$, for the following lengths:

$L_n = L_p = 400 \text{ nm}$

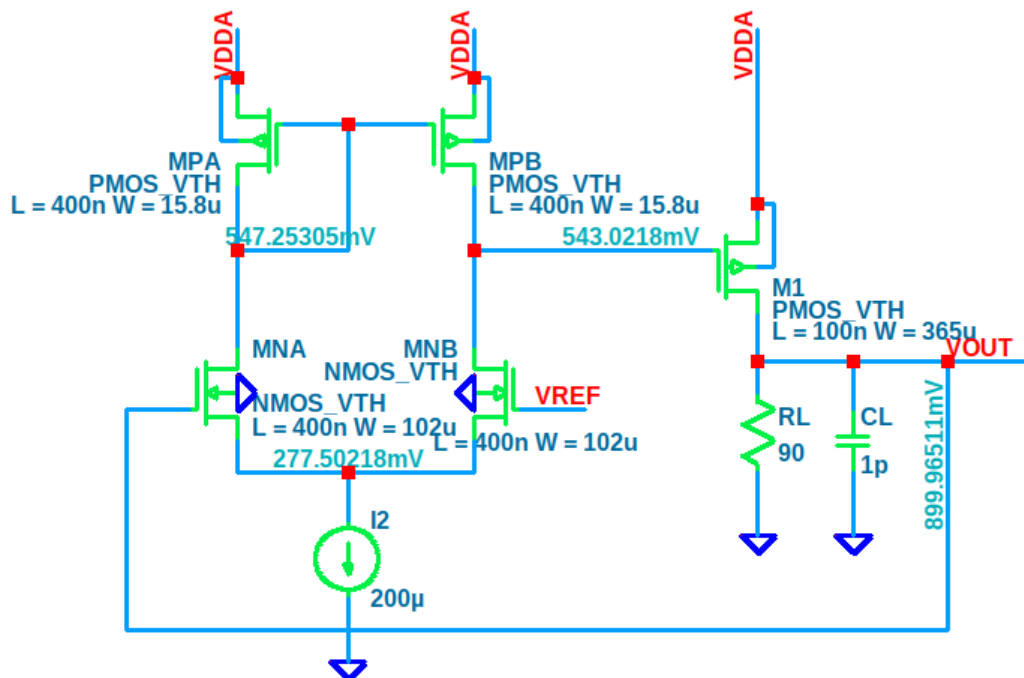


Figure 4: low-frequency analysis - final circuit without bias

SPICE Analysis

	VS(mV)	VD(mV)	A1	Aa
--	--------	--------	----	----

Analysis	0.27	0.547	6.8	164.82
SPICE	0.277	0.543	6.78	163.29

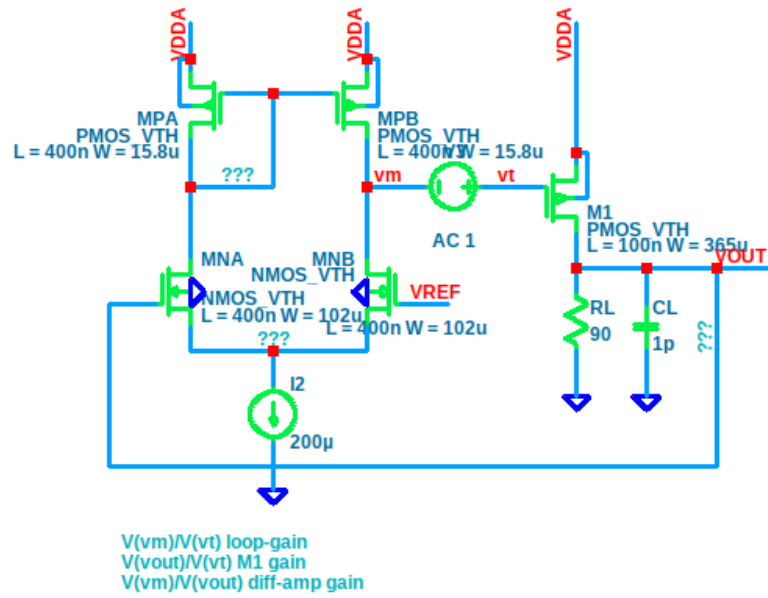


Figure 5: TB AC analysis

high-frequency analysis

$$ao = G_{m1} R_1 G_{m2} R_2$$

$$\frac{1}{\omega_{pd}} = R_1 (G_{m2} R_2) C_c$$

$$f_{p2} = \frac{G_{m2}}{2\pi C_L}$$

$$\frac{1}{\omega_{zp}} = \frac{C_c}{G_{m2}}$$

if we are using dominant pole compensations with Miller C_c

where $R_1 = 1/g_{dsa}$ output resistance of the differential amplifier

and $R_2 = 1/(Y_L + g_{ds1})$ the resistance at the output node

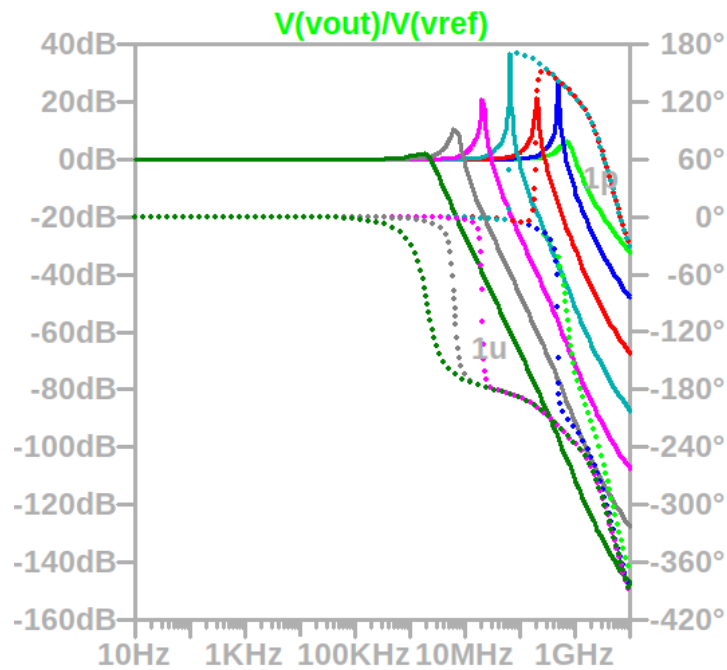


Figure 6: Closed-loop frequency response as CL is varied from 1pF to 1uF

From Figure 6 we can see that, when CL is very small or very large, the LDO behaves like a first-order circuit, but when the two poles get close, the amplifier behaves like a second-order system that has poor phase margin.

In the loop-gain AC analysis in Figure 7 we can see a complex-zero determined by the transfer-function of the differential amplifier Figure 8.

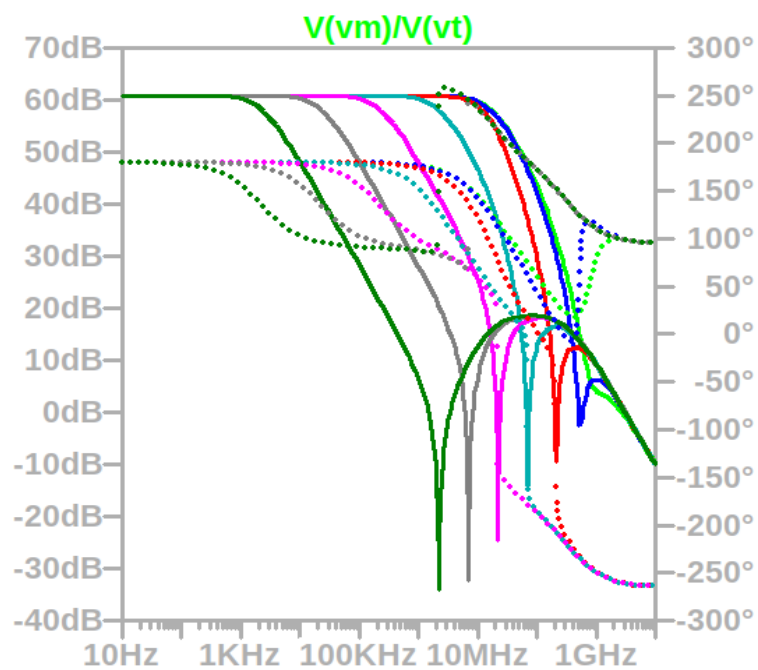


Figure 7: loop-gain

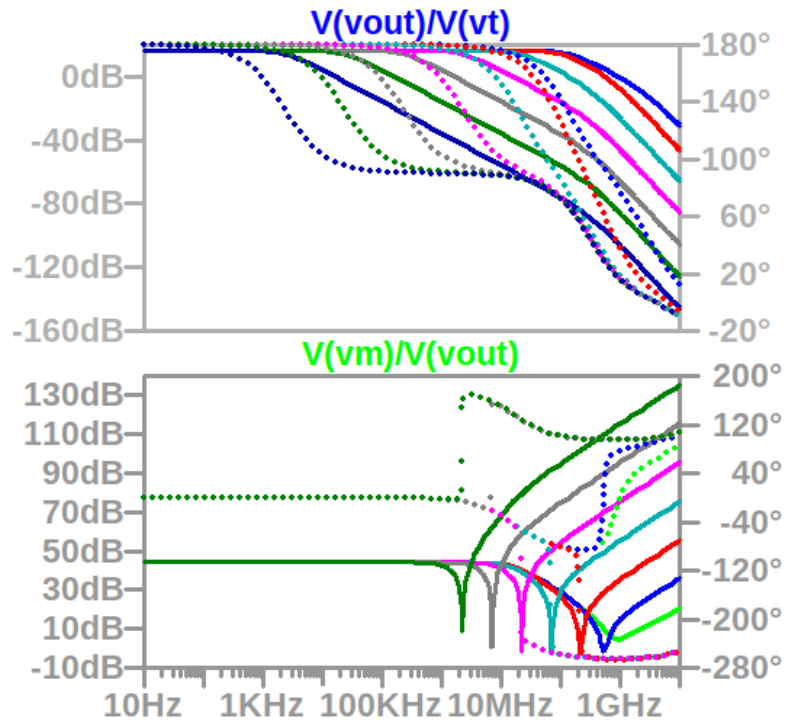


Figure 8: Top-to-bottom CS M1, and the differential amplifier transfer functions respectively

For example with $C_L = 10\text{pF}$, and Miller capacitor across drain-gate of M1, $C_c = 1\text{pF}$ our regulator loop-gain is inherently stable, Figure 9.

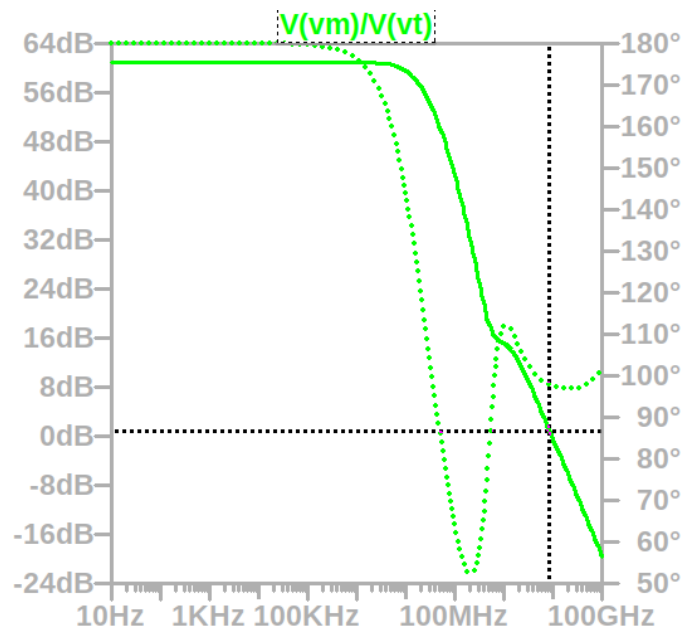


Figure 9: loop-gain

 


Figure 10: load-regulation, I step 0.1mA to 10mA

Bibliography

1. <https://github.com/bmurmman/Book-on-gm-ID-design>

Note that the functions from [1] are not compatible with this note's design, as I generated my own LUT for the PDK45 with NGSPICE and I also had to modify the functions to work with it, as the original paper requires access to Cadence Virtuoso and Matlab.